



Stellenbosch

UNIVERSITY
IYUNIVESITHI
UNIVERSITEIT

E344 Assignment 1

Sean Muller

23575786

Report submitted in partial fulfilment of the requirements of the module
Design (E) 344 for the degree Baccalaureus in Engineering in the Department of Electrical
and Electronic Engineering at Stellenbosch University.

July 31, 2022

Plagiaatverklaring / *Plagiarism Declaration*

1. Plagiaat is die oorneem en gebruik van die idees, materiaal en ander intellektuele eiendom van ander persone asof dit jou eie werk is.

Plagiarism is the use of ideas, material and other intellectual property of another's work and to present it as my own.

2. Ek erken dat die pleeg van plagiaat 'n strafbare oortreding is aangesien dit 'n vorm van diefstal is.

I agree that plagiarism is a punishable offence because it constitutes theft.

3. Ek verstaan ook dat direkte vertalings plagiaat is.


I also understand that direct translations are plagiarism.

4. Dienooreenkomstig is alle aanhalings en bydraes vanuit enige bron (ingesluit die internet) volledig verwys (erken). Ek erken dat die woordelike aanhaal van teks sonder aanhalingstekens (selfs al word die bron volledig erken) plagiaat is.

Accordingly all quotations and contributions from any source whatsoever (including the internet) have been cited fully. I understand that the reproduction of text without quotation marks (even when the source is cited) is plagiarism

5. Ek verklaar dat die werk in hierdie skryfstuk vervat, behalwe waar anders aangedui, my eie oorspronklike werk is en dat ek dit nie vantevore in die geheel of gedeeltelik ingehandig het vir bepunting in hierdie module/werkstuk of 'n ander module/werkstuk nie.

I declare that the work contained in this assignment, except where otherwise stated, is my original work and that I have not previously (in its entirety or in part) submitted it for grading in this module/assignment or another module/assignment.

23575786	
Studentenommer / <i>Student number</i>	Handtekening / <i>Signature</i>
S. Muller	July 31, 2022
Voorletters en van / <i>Initials and surname</i>	Datum / <i>Date</i>

Contents

Declaration	i
List of Figures	iii
List of Tables	iv
Nomenclature	v
1. Literature survey	1
1.1. Operational amplifiers	1
1.2. Current sensing	3
2. Detail design	4
2.1. Current sensor	4
2.1.1. Opamp configuration	4
2.1.2. Opamp design	4
3. Results	5
3.1. Current sensor	5
3.1.1. Simulation	5
3.1.2. Practical	6
3.1.3. Circuit	7
Bibliography	8
A. Social contract	9
B. GitHub Activity Heatmap	10

List of Figures

1.1. Circuit diagrams of 4 op amp configurations	2
2.1. Current sensing circuit design	4
3.1. Current sensing circuit simulation results	5
3.2. Circuit response to different input conditions	6
3.3. Labelled circuit and student card.	7

List of Tables

Nomenclature

Variables and functions

R_{sense} Resistor used to in series with the load to measure current

Acronyms and abbreviations

op amp Operational amplifier

Chapter 1

Literature survey

This chapter will cover a review on the different methods for current sensing and the limitations, considerations and configurations for operational amplifier design for current sensing.

1.1. Operational amplifiers

Operational amplifiers: limitations and considerations

There are many practical limitations to operational amplifiers in comparison to the ideal model. The limit on the common mode voltage is a concern as the limit is usually around the rail voltage and since the negative rail will be ground and the common mode voltage will be close to 0 the data sheet should be consulted to ensure normal operation of the op amp [1].

A significant consideration is the offset voltage between the inputs of the opamp as when the inputs are equal (no current is being given to the load) there will be an offset voltage on the order of mV which is a similar magnitude to the relevant voltages [2]. This will result in significant output voltages at no load. However a negative feedback will greatly reduce the impact of input offset voltage and current [2].

The output voltage won't be able to go all the way to the rail voltages. Therefore there will be some output voltage when there is no current through the load due to the output not able to go below a certain voltage above ground.

Operational amplifier configurations


There are many different configurations for operational amplifiers, this section will cover 4 basic configurations that could be useful for the current sensor.

The simplest circuit is the voltage follower, it requires no other components and causes the output voltage to track the input voltage. The op amp in this configuration provides a large input impedance and very low output impedance which can allow signals to pass between logic components without them loading each other and can be used to stabilize a voltage divider [3].

The inverting op amp is a configuration where the output is connected to the inverting input terminal using a resistor, there is a second resistor connecting this terminal to the circuit input. The non-inverting input is connected to ground. This configuration results in a gain equal to the negative of the ratio between the two resistors. The negative gain cause the output to be exactly out of phase with the input [3].


The non-inverting op amp configuration is similar to the inverting amplifier except the input is connected directly to the non-inverting input and the inverting input terminal has a resistor connecting it to the ground. This results in the gain being equal to 1 plus the ratio between the two resistors [3].

The differential amplifier is similar to the inverting amplifier, but instead of connecting the non-inverting input to ground a second signal is connected to the input of this terminal through a resistor of the same value as the other terminal. This results in the output being the difference between the two signals scaled by the ratio of the feedback resistor to the input resistor. This configuration is good at filtering out noise common to both input terminals [3].

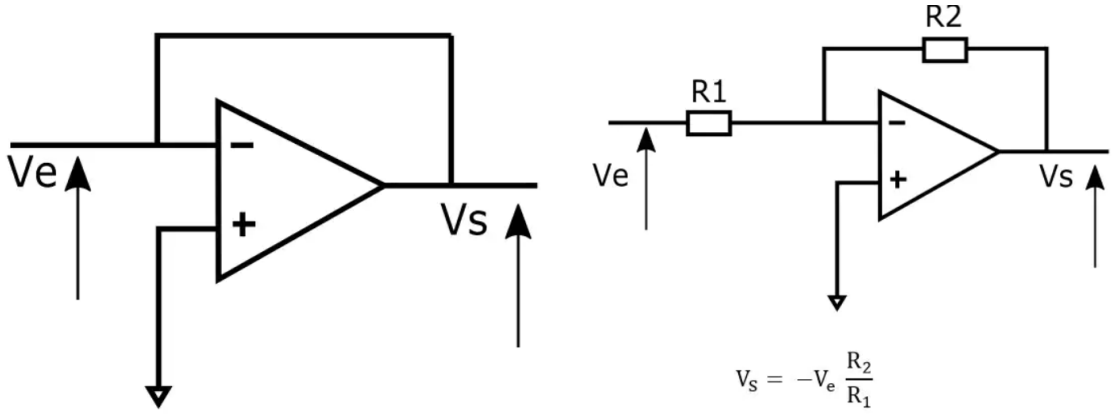

(a) Circuit diagram for a voltage follower [3]

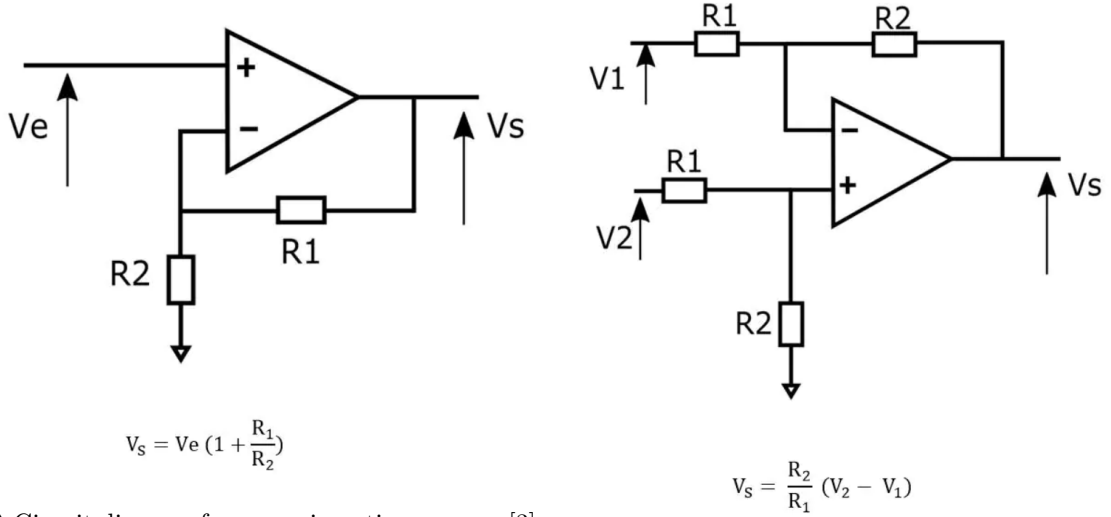(b) Circuit diagram for a inverting op amp [3].



(c) Circuit diagram for a non-inverting op amp [3]

(d) Circuit diagram for a differential op amp [3]

Figure 1.1: Circuit diagrams of 4 op amp configurations

1.2. Current sensing

There are many different techniques to measure current. Both invasive and non invasive methods each with their own advantages and disadvantages that make them suitable for different situations. An invasive current sensor negatively affect the system and decreases performance whereas a non-invasive current sensor doesn't affect the operation of the system at a meaningful level.

Hall effect

The Hall effect current sensor is a non invasive method of current sensing that uses the magnetic field generated around a current carrying conductor [4]. This magnetic field creates a voltage across the material of the sensor. Hall effect sensors measure this voltage to determine the current flowing in a conductor [5]. There are many advantages to using a Hall effect sensor however, besides the amplifier circuit additional circuits are required and is more costly than other measurement methods [4].

Rogowski coil

The Rogowski coil is a non invasive current sensing method that uses a helical shaped coil that is wrapped around the conductor that you want to measure current in. The coil outputs a voltage depending on the rate of change of current through the conductor, this requires an integrator circuit to create an output voltage that is proportional to the current. The Rogowski coil is very useful for high frequency currents and does not require complex temperature compensation. However this method is only suitable for AC current [4].

Shunt Resistor

The shunt resistor is the most common current sensing technique and uses a resistor in series with the current to be measured. This is a invasive current measuring method. The shunt resistor produces a voltage drop proportional to the current, however the resistance and hence the voltage must be kept low in order to reduce the power consumption. This requires a high gain amplifier circuit to increase the small voltages to meaningful levels. The shunt resistor is a very cost effective solution that works on both AC and DC however it creates a decrease in system efficiency and can't handle high currents due to power dissipation across the resistor. Thermal drift also results in error [4].

High-side vs low-side current sensing is only applicable for invasive methods like the shunt resistor. Low-side has the advantages of being simple and low cost and low input common mode voltage however it can't detect high current due to a short [6]. High-side current sensing removes the ground disturbance and can detect accidental shorts however it has a higher complexity and cost because the gain circuit must be able to handle high common mode voltages [6].

Chapter 2

Detail design

2.1. Current sensor

Currently being rewritten.

2.1.1. Opamp configuration

2.1.2. Opamp design

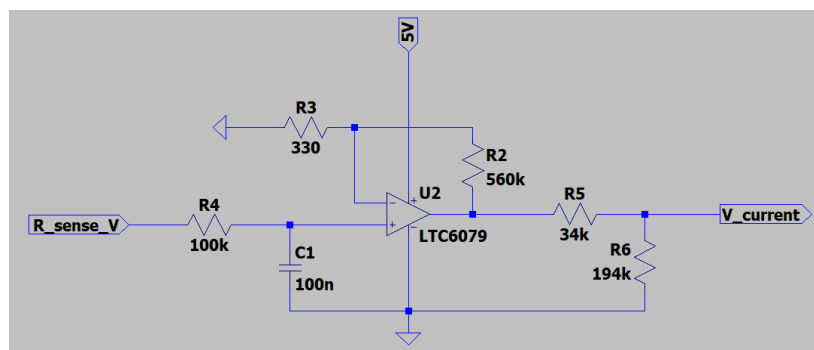


Figure 2.1: Current sensing circuit design


Chapter 3

Results


3.1. Current sensor

3.1.1. Simulation


Figure 3.1 shows the simulation results for the circuit shown in Figure: 2.1. The requirement for a 10 mV signal at 1 kHz to result in less than 250 mV at the output, is shown to be met in 3.1a where the 10 mV signal at 1 kHz results in an output of ≈ 160 mV. Figure 3.1b shows that the circuit has a response time less than 100ms, with a response time of ≈ 30 ms. The requirement that the amplification circuit draws less than 150 μ A is met in Figure: 3.1c where the maximum current draw is 83 μ A.

 

 (a) Noise input vs output of current sensing circuit.



 (b) Step response of current sensing circuit.



(c) Current draw of 5V supply to current sensing circuit.

Figure 3.1: Current sensing circuit simulation results

3.1.2. Practical

As shown in Figure:3.2 the practical results match the simulated results shown in Figure: 3.1.


The practical response to no input (3.2a) shows an output of 66 mV, this differs from the simulation output of 0 V due to the non ideal nature of practical op amps and is due to the offset voltage between the input terminals.

Figure: 3.1b shows an output voltage of 2.2 V to a 200 mA input while Figure: 3.2c shows a 1.82 V output to a 200 mA input. This is due to the practical circuit having a reduced gain in comparison to the simulation. This was done to reduce the affect of the input offset voltage mentioned previously.


Figure: 3.2d shows the output clips sat 3.28 V which is very close to the theoretical 3.3 V.

Figure: 3.2e shows a lesser response to noise than the simulation, this is due to the noise input to the practical circuit is different to the simulated noise and at a higher frequency so the low pass filter attenuates it more heavily.

 
The measure response time in Figure: 3.2f is 24 ms which is very close to the response time measured in the simulation of 30 ms.




(a) Circuit response to no input.

 

 
(b) Circuit response to free running motor.



 
(c) Circuit response to slight restriction on the motor.



(d) Circuit response to motor stall.

 

(e) Circuit response to noise.

 

(f) Circuit response to step input.

Figure 3.2: Circuit response to different input conditions

3.1.3. Circuit



Figure 3.3: Labelled circuit and student card.

Bibliography

- [1] R Nave, “Departures from ideal op-amp.” [Online]. Available: <http://hyperphysics.phy-astr.gsu.edu/hbase/Electronic/opamprac.html>
- [2] University of Ottawa, “Physical limitations of op amps.” [Online]. Available: <https://www.site.uottawa.ca/~rhabash/ELG3336DCImperfections.pdf>
- [3] Jean Jacques Meneu, “Top 10 fundamental op amp circuits,” 2016. [Online]. Available: <https://www.arrow.com/en/research-and-events/articles/fundamentals-of-op-amp-circuits>
- [4] Current Sensing Techniques using Different Current Sensors, “How to make opamps amp op,” 2019. [Online]. Available: <https://circuitdigest.com/article/how-to-measure-current-in-a-circuit-with-different-current-sensing-techniques>
- [5] RS Electronics, “The guide to hall effect sensors.” [Online]. Available: <https://za.rs-online.com/web/generalDisplay.html?id=ideas-and-advice/hall-effect-sensors-guide>
- [6] Preeti Jain, “Current sensors.” [Online]. Available: <https://www.engineersgarage.com/current-sensors/>

Appendix A

Social contract



UNIVERSITEIT • STELLENBOSCH • UNIVERSITY
jou kennisvenoot • your knowledge partner

E-design 344 Social Contract

2022

The purpose of this document is to establish commitment between the student and the organisers of E344. Beyond the commitment made here, it is not binding.

In the months preceeding the term, the lecturer (Thinus Booysen) and a few paid helpers (Rita van der Walt, Keegan Hull, and Michael Ritchie) spent countless hours to prepare for E344 to ensure that you get your money's worth, that you are enabled to learn from the module, and demonstrate and be assessed on your skills. We commit to prepare the assignments, to set the assessments fairly, to be reasonably available, and to provide feedback and support as best and fast we can. We will work hard to give you the best opportunity to learn from and pass analogue electronic design E344.

I, have registered for E344 of my own volition with the intention to learn of and be assessed on the principals of analogue electronic design. Despite the potential publication online of supplementary videos on specific topics, I acknowledge that I am expected to attend the scheduled lectures to make the most of these appointments and learning opportunities. Moreover, I realise I am expected to spend the additional requisite number of hours on E344 as specified in the yearbook.

I acknowledge that E344 is an important part of my journey to becoming a professional engineer, and that my conduct should be reflective thereof. This includes doing and submitting my own work, working hard, starting on time, and assimilating as much information as possible. It also includes showing respect towards the University's equipment, staff, and their time.

Prof. MJ (Thinus) Booysen

Student number:

Signature: Signature:

Date: Date:

Appendix B

GitHub Activity Heatmap

